 


# Fundamentals of Computer Science (MCAC-0017)

## COMBINATIONAL CIRCUITS




# Overview

- Introduction to Combinational Circuits
- Adder
- Ripple Carry Adder
- Subtraction
- Adder/Subtractor

# Combinational Circuits


Digital logic circuits are basically categorized into two types:

 1. Combinational circuits in which there are no feedback paths from outputs to inputs and there is no memory.
2. Sequential circuits in which feedback paths exist from outputs


 
# Binary addition by hand

- You can add two binary numbers one column at a time starting from the right, just like you add two decimal numbers.
- But remember it's binary. For example,  $1 + 1 = 10$  and you have to carry!



# Adder

- Design an Adder for 2-bit numbers?
- **1. Specification:**
  - 2 inputs (X,Y)
  - 2 outputs (C,S)

# Adder

- Design an Adder for 2-bit numbers?
- **1. Specification:**  
2 inputs (X,Y)  
2 outputs (C,S)
- **2. Formulation:**

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Adder

- Design an Adder for 2-bit numbers?

- **1. Specification:**


2 inputs (X,Y)

2 outputs (C,S)

- **2. Formulation:**

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


- **3. Optimization/Circuit**

 

# Half Adder

- This adder is called a Half Adder
- **Q: Why?**

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 



# Full Adder

- A combinational circuit that adds 3 input bits to generate a Sum bit and a Carry bit
- A truth table and sum of minterm equations for C and S are shown below.

	X	Y	Z	C	S
	0	0	0	0	0
	0	0	1	0	1
	0	1	0	0	1
$0 + 1 + 1 = 10$ →	0	1	1	1	0
	1	0	0	0	1
	1	0	1	1	0
	1	1	0	1	0
$1 + 1 + 1 = 11$ →	1	1	1	1	1

$$C(X,Y,Z) = \sum m(3,5,6,7)$$

$$S(X,Y,Z) = \sum m(1,2,4,7)$$

# Full Adder

- A combinational circuit that adds 3 input bits to generate a Sum bit and a Carry bit

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Sum

X \ YZ	YZ			
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$S = X'Y'Z + X'YZ' + XY'Z' + XYZ$$

$$= X \oplus Y \oplus Z$$

Carry

X \ YZ	YZ			
	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$C = XY + YZ + XZ$$

# Full Adder = 2 Half Adders

**Manipulating the Equations:**

$$S = X \oplus Y \oplus Z$$

$$C = XY + XZ + YZ$$

# Full Adder = 2 Half Adders

## Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$

$$C = XY + XZ + YZ$$

$$= XY + XYZ + XY'Z + X'YZ + \cancel{XYZ}$$

$$= XY(1 + Z) + Z(XY' + X'Y)$$

$$= XY + Z(X \oplus Y)$$


# Full Adder = 2 Half Adders

## Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$

$$C = XY + XZ + YZ = XY + Z(X \oplus Y)$$

Think of  
Z as a  
carry in

 

Src: Mano's Book

# Bigger Adders

- How to build an adder for  $n$ -bit numbers?
  - Example: 4-Bit Adder
    - Inputs ?
    - Outputs ?
    - What is the size of the truth table?
    - How many functions to optimize?

# Bigger Adders

- How to build an adder for n-bit numbers?
  - Example: 4-Bit Adder
    - Inputs ? 9 inputs
    - Outputs ? 5 outputs
    - What is the size of the truth table? 512 rows!
    - How many functions to optimize? 5 functions

# Ripple Carry Adder


- To add n-bit numbers:
  - Use n Full-Adders in parallel
  - The carries propagates as in addition by hand
  - Use Z in the circuit as a  $C_{in}$

- |       |   |   |   |
|-------|---|---|---|
| 1     | 0 | 0 | 0 |
| 0     | 1 | 0 | 1 |
| 0     | 1 | 1 | 0 |
| <hr/> |   |   |   |
| 1     | 0 | 1 | 1 |
- 
- 
-


 
# Binary Parallel Adder

- To add n-bit numbers:
  - Use n Full-Adders in parallel
  - The carries propagate as in addition by hand



Src: Mano's Book


This adder is called *ripple carry adder*

# Subtraction (2's Complement)

- How to build a subtractor using 2's complement?
 
# Subtraction (2's Complement)

- How to build a subtractor using 2's complement?




Src: Mano's Book

$$S = A + (-B)$$

# Adder/Subtractor

- How to build a circuit that performs both addition and subtraction?

# Adder/Subtractor

 

Src: Mano's Book

Using full adders and XOR we can build an Adder/Subtractor!


# Decoders

- A decoder is a combinational circuit that converts binary information from the  $n$  coded inputs to a maximum of  $2^n$  unique outputs.
- The decoders presented are called  $n$ -to- $m$  line decoders, where  $m \leq 2^n$ . Their purpose is to generate the  $2^n$  (or fewer) binary combinations of the  $n$  input variables. A decoder has  $n$  inputs and  $m$  outputs and is also referred to as an  $n \times m$  decoder


 
# 2 to 4 line decoder

- In the 2 to 4 line decoder, there is a total of three inputs, i.e.,  $A_0$ ,  $A_1$  and  $E$  and four outputs, i.e.,  $Y_0$ ,  $Y_1$ ,  $Y_2$ , and  $Y_3$ . For each combination of inputs, when the enable ' $E$ ' is set to 1, one of these four outputs will be 1.
- **Block Diagram**



# Truth Table

Enable	INPUTS		OUTPUTS			
E	A <sub>1</sub>	A <sub>0</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

The logical expression of the term Y0, Y0, Y2, and Y3 is as follows:

$$Y_3 = E \cdot A_1 \cdot A_0$$


$$Y_2 = E \cdot A_1 \cdot A_0'$$

$$Y_1 = E \cdot A_1' \cdot A_0$$

$$Y_0 = E \cdot A_1' \cdot A_0'$$



 Logical circuit of the above expressions is given below:




# Applications of Decoders

- They may be used to route input data to a specified output line for example addressing for memory.
- Decoders are used in audio systems to convert analogue audio into digital data.
- Used as a decompressor to convert compressed data like images and videos into decompressed form.
- Decoders are also used as building blocks in implementing arbitrary switching functions.
 
# Encoders

- An encoder is a digital circuit that performs the inverse operation of a decoder. An encoder has  $2^n$  (or less) input lines and  $n$  outputs lines. The output lines generate the binary code corresponding to the input value.
- An example of an encoder is the octal-to-binary encoder.



Block diagram of encoder

TABLE 2-2 Truth Table for Octal-to-Binary Encoder

Inputs								Outputs		
$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

- The encoder can be implemented with three OR gates.

# Multiplexer (Data Selectors)

- ❑ The term Multiplexer means many into one.
- ❑ Multiplexing is the process of transmitting a large number of information over a single line.
- ❑ A Digital Multiplexer (MUX) is a combinational Circuit that select one digital information from several sources and transmits the selected information on a single output line.
- ❑ A Multiplexer is also called a Data Selector.
- ❑ The Multiplexer has several data input line and a single output line.

## Cont.

□ MUX directs one of the inputs to its output line by using a control bit word (*selection line*) to its *select lines*.

□ Multiplexer contains the followings:

❖ data inputs


❖ selection inputs

❖ a *single output*


□ Selection input determines the input that should be connected to the output.

□ The multiplexer acts like an electronic switch that selects one from different.

# Block diagram of Multiplexer

 


# 4 to 1 Multiplexer Logic Symbol

 



## 4 to 1 Multiplexer Logic diagram

 

## Cont.,

- To demonstrate the operation of the circuit, consider the case when  $S_1 S_0 = 00$ .
- If  $S_1 S_0 = 00$  is applied to the select lines, the AND gate associated with  $D_0$  will have two of its input equal to 1 and the third input connected to  $D_0$ .
- The other three AND gates have 0 in at least one of their inputs, which make their output equal to 0.
- Hence, the OR output ( $Y$ ) is equal to the value of  $D_0$ .

## Cont.,

- Thus, it provides a path from the selected input and the data on the input  $D_0$  appears on the data-output line (Y).
- If  $S_1 S_0 = 01$  (binary 1) applied to the select lines , the data on the input  $D_1$  appears on the data output line.

## Cont.,

- If  $S_1 S_0 = 10$  (binary 2) is applied, the data on the input  $D_2$  appears on the output line (Y).
- Similarly, if  $S_1 S_0 = 11$  is applied, the data on  $D_3$  is switched to the output line (Y).
- The AND gates and the inverters resemble a decoder circuit, and indeed they decode the input select lines.
- In general, a  $2^n$ -to-1 multiplexer is constructed from  $n$ -to- $2^n$  decoder by adding to it  $2^n$  input lines, one each AND gate.


## Cont.,

- The output of the AND gates are applied to a single OR gate to provide a single output.
- The size of the multiplexer is specified by the number  $2^n$  of input lines and the single output line.
- Multiplexer ICs have an enable input to control the operation of the unit.
- The enable input (also called strobe) can be used to cascade two or more multiplexer ICs to construct a multiplexer with larger number of inputs

# Truth table of 4-to-1 Multiplexer

Data select inputs		Output
S <sub>1</sub>	S <sub>0</sub>	Y
0	0	D <sub>0</sub>
0	1	D <sub>1</sub>
1	0	D <sub>2</sub>
1	1	D <sub>3</sub>

# 8-1 Multiplexer Circuit

 


# De-Multiplexer


- The De-Multiplexer is a combinational logic circuit that performs the reverse operation of multiplexer (Several output lines, one input line).
- De -Multiplexer means one to many. A De-Multiplexer is a circuit with one input and many output. By applying control signal, we can steer any input to the output. Few types of De -Multiplexer are 1-to 2, 1-to-4, 1-to-8 and 1-to 16 De -Multiplexer .
- De-Multiplexer is the process of taking information from one input and transmitting the same over one of several outputs.




# Block diagram of DeMultiplexer

 

# 1 to 4 DeMultiplexer Logic Symbol

 

## 1 to 4 DeMultiplexer Logic diagram

 

# Truth Table of 1 to 4 DeMultiplexer

Data Input	Select Inputs		Output			
D	S <sub>1</sub>	S <sub>0</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
D	0	0	0	0	0	D
D	0	1	0	0	D	0
D	1	0	0	D	0	0
D	1	1	D	0	0	0

Thankyou

Any Query

?